

## **Elec Eng 2EI5**

### **Design Project #3**

#### ***Problem Statement***

Design, simulate, and build an amplifier that can take an input of  $\pm 0.5\text{V}$  from a source with an internal resistance of  $100\Omega$  and deliver it to a  $100\Omega$  load with good linearity and less than 10% attenuation.

#### ***Test Requirements***

1. You are limited to the dc supplies available from your Digilent module.
2. You are limited to a single transistor (MOSFET or BJT).
3. You are limited to the components in your lab kit.
4. You may not use op-amps for this project.
5. In testing your circuit you should feed the input into the circuit from your Digilent function generator through a  $100\Omega$  resistor that you connect in series with the function generator. You should demonstrate different waveforms from the function generator. You should demonstrate different amplitudes up to  $\pm 0.5\text{V}$ . You should demonstrate a range of frequencies.
6. You should be able to answer questions about:
  - a. Choice of circuit
  - b. Choice of transistor
  - c. How the circuit works
  - d. Design tradeoffs, if any, and choice of component values

#### ***Report Requirements***

Your submitted report should not exceed four pages. You are allowed:

1. A maximum of 2 pages showing your hand analysis and discussing design considerations;
2. A maximum of 1 page showing figures (circuit diagram, simulation results, etc.); and
3. A maximum of 1 page describing your simulations, reporting results measured in the lab, and comparing theory with experiment.

At a minimum, your report must include:

1. A picture of your physical circuit;
2. A schematic of your circuit;
3. Screen captures of your measurements;
4. The PSpice netlist for your circuit; and
5. Screen captures of your PSpice simulations.

You are expected to explain in your report:

1. Hand design
  - a. Why did you choose a specific circuit topology?
  - b. Why did you choose a specific device (MOSFET or BJT)?
  - c. How did you estimate needed component values for your circuit?

- d. How did you calculate or choose component values to meet the specifications?
  - e. How did you address all of the specifications that are given here?
- 2. Simulations
  - a. What simulations did you choose to perform?
  - b. What Spice models did you have to use and how did you obtain parameters for those models?
  - c. How do the results of simulation compare with hand design?
- 3. Measurement
  - a. What measurements did you perform on your circuit?
  - b. Did the circuit meet specifications? Justify your answer using the specific measurements you took.
  - c. Explain any discrepancies between your hand calculations, Spice simulations, and measurements.
  - d. If the circuit you built did not meet specifications, can you address why that happened? Having done the project and demonstrated a circuit, have you come to understand what circuit(s) could meet the specifications?

### ***Marking***

Rubrics for marking will be published on Avenue. Please check them for more guidance.

### ***Workload & Time Management***

In order to successfully complete this project you will need to learn about:

- 1. Different amplifier topologies and what each topology is useful for;
- 2. How to experimentally characterize an amplifier circuit to completely describe its behavior; and
- 3. How to simulate amplifier circuits to be able to understand the effect of different design choices (including component values).

The first two items are the subject of Module 6 in the course and are covered in the textbook in Chapter 7. The last item is covered in the Lab Manual available on Avenue.